

EE230: Experiment 3

Schmitt Trigger, Monostable, and Astable Circuits

Hitesh Kandala, 180070023

February 11, 2020

1 Overview of the experiment

1.1 Aim of the experiment

- Design the circuit of Schmitt Trigger and compare the threshold voltages V_{TH} and V_{TL} with the values you expect theoretically.
- Wire up the circuit of astable multivibrator and compare the minimum and maximum period of oscillation with your calculation.
- Wire up the circuit of monostable multivibrator and measure the duration of the output pulse. Compare it with your calculation.

1.2 Theory

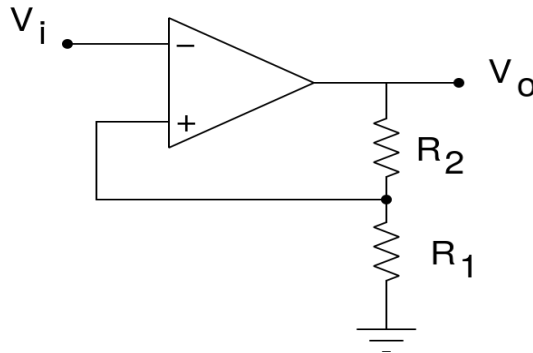


Figure 1: Schmitt trigger

When V_i is sufficiently large, the output voltage V_o of the circuit (known as the “Schmitt trigger”) is V_{sat} as shown in Fig. 1. The voltage at the non-inverting input terminal of the op amp V_+ (with respect to ground) is then $V_+ \equiv V_{TL} = V_{sat} \times (\frac{R_1}{R_1+R_2})$. As V_i is reduced and becomes smaller than V_{TL} , the op amp output changes from $-V_{sat}$ to $+V_{sat}$ (since $V_- < V_+$). Now, V_+ is equal to $V_+ \equiv V_{TH} = +V_{sat} \times (\frac{R_1}{R_1+R_2})$. If V_i is reduced further, this state of affairs continues to hold. If V_i is increased, the output flips when V_i crosses V_{TH} .

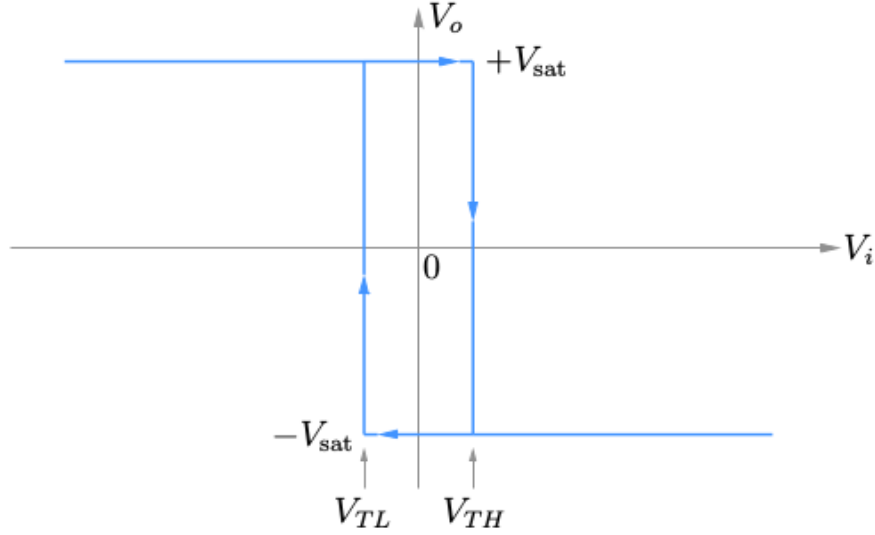


Figure 2: V_o versus V_i relationship for Schmitt trigger

The Schmitt trigger is a comparator with hysteresis (or “memory”). Since the input threshold voltage (V_{TH} or V_{TL}), at which the output flips, depends on the “state” of the circuit. Note that the high and low threshold voltages, V_{TH} and V_{TL} , respectively, are symmetric about 0 V for the Schmitt trigger circuit i.e., $V_{TH} = V_{TL}$. By connecting a DC voltage source V_a , we can make them asymmetric (see Fig. 3), as shown below.

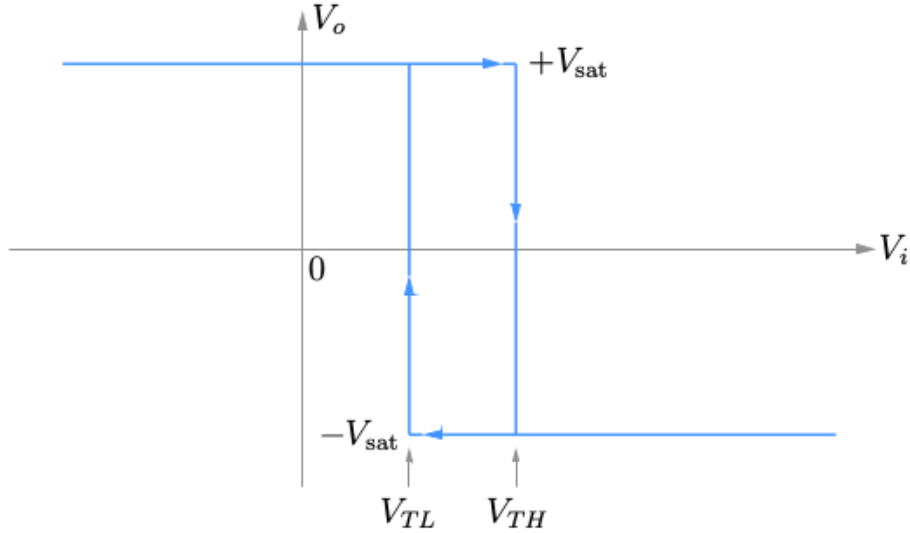


Figure 3: V_o versus V_i relationship for the asymmetric Schmitt trigger

When V_o is $+V_{sat}$, we have

$$V_+ = +V_{sat} \frac{R_1}{R_1 + R_2} + V_a \frac{R_2}{R_1 + R_2} \quad (1)$$

since the current entering the non-inverting input of the op amp can be neglected. Similarly, when V_o is V_{sat} , we have

$$V_+ = -V_{sat} \frac{R_1}{R_1 + R_2} + V_a \frac{R_2}{R_1 + R_2} \quad (2)$$

The output voltage of the Schmitt trigger can be limited by using a Zener pair as shown in Fig. 4. Let the breakdown voltage of the Zener diode be V_Z and the turn-on voltage be V_{on} . Consider the op amp output V_{o1} to be $+V_{sat}$. Because of the diode pair, the output voltage V_o gets limited to $V_{on} + V_Z$, with D_1 in forward conduction, and D_2 in reverse breakdown.

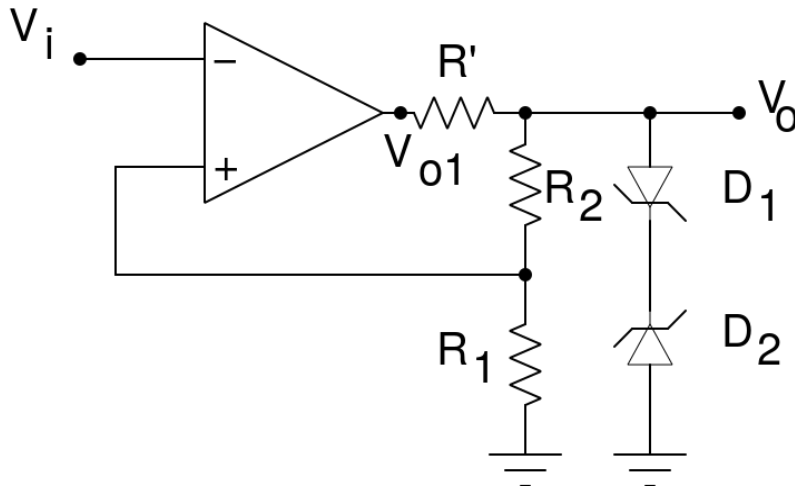


Figure 4: Schmitt trigger circuit with V_o limited to $(V_Z + V_{on})$

Note that the difference between V_{o1} and V_o appears across the resistor R which must be chosen to limit the op amp output current to a reasonable value (a few mAs). Connecting the diode pair directly to the op-amp output would lead to unhealthy events. In a similar manner, when V_{o1} is V_{sat} , the output voltage V_o gets limited to $(V_{on} + V_Z)$, with D_2 in forward conduction, and D_1 in reverse breakdown.

2 Experimental results

2.1 Schmitt trigger

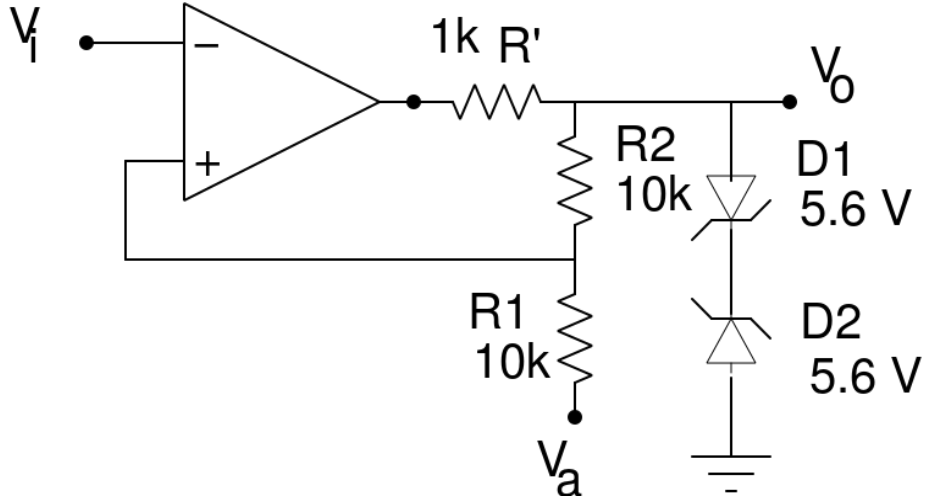


Figure 5: Schmitt trigger

(A) With $V_a = 0V$:

$$V_{TL} = -V_{sat} \times \left(\frac{R_1}{R_1 + R_2} \right) \quad (3)$$

$$V_{TH} = +V_{sat} \times \left(\frac{R_1}{R_1 + R_2} \right) \quad (4)$$

The actual resistance of resistors shown in fig 5 are, $R_1 = 9.7k$, $R_2 = 9.82k$, $R' = 0.96k$
Drop across zener diodes is $V_Z + V_{ON} = 5.6V + 1.12V = 6.72V$

$$V_{TL} = -6.72 \times \left(\frac{9.7}{9.7 + 9.82} \right) \quad (5)$$

$$\boxed{V_{TL} = -3.34V} \quad (6)$$

Similarly,

$$\boxed{V_{TH} = +3.34V} \quad (7)$$

Hence, theoretical values of V_{TH} and V_{TL} are **+3.34V** and **-3.34V** respectively.

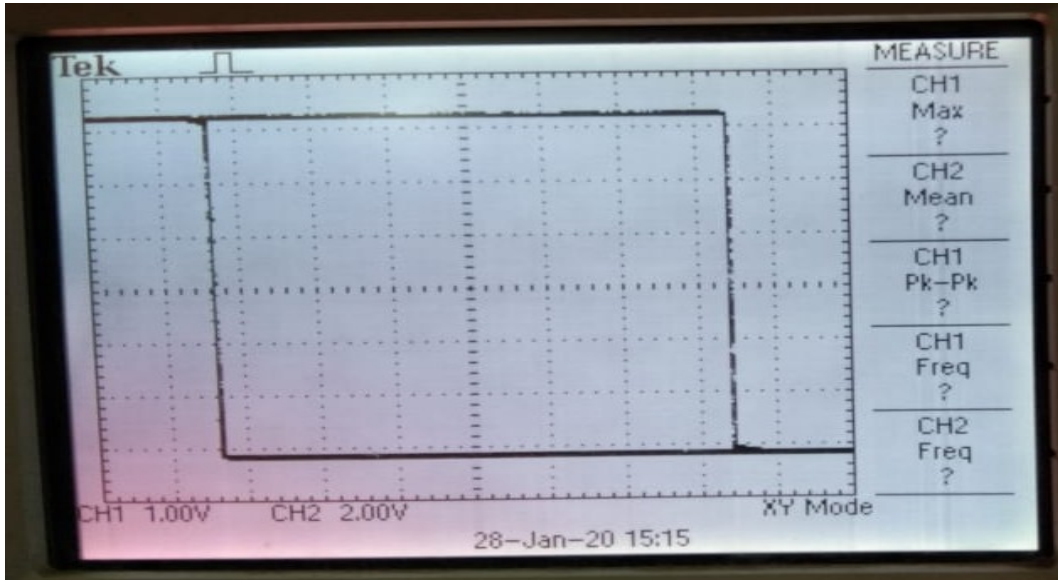


Figure 6: V_o versus V_i relationship for $V_a = 0V$

The observed value of $V_{TH} = +3.4V$ and $V_{TL} = -3.4V$

(B) With $V_a = 3V$:

$$V_{TL} = -V_{sat} \times \left(\frac{R_1}{R_1 + R_2} \right) \quad (8)$$

$$V_{TH} = +V_{sat} \times \left(\frac{R_1}{R_1 + R_2} \right) \quad (9)$$

The actual resistance of resistors shown in fig 5 are, $R_1 = 9.7k$, $R_2 = 9.82k$, $R' = 0.96k$
Drop across zener diodes is $V_Z + V_{ON} = 5.6V + 1.12V = 6.72V$

$$V_{TL} = -6.72 \times \left(\frac{9.7}{9.7 + 9.82} \right) + 3 \times \left(\frac{9.82}{9.7 + 9.82} \right) \quad (10)$$

$$\boxed{V_{TL} = -1.83V} \quad (11)$$

Similarly,

$$V_{TH} = 6.72 \times \left(\frac{9.7}{9.7 + 9.82} \right) + 3 \times \left(\frac{9.82}{9.7 + 9.82} \right) \quad (12)$$

$$\boxed{V_{TH} = +4.85V} \quad (13)$$

Hence, theoretical values of V_{TH} and V_{TL} are $+4.85V$ and $-1.83V$ respectively.

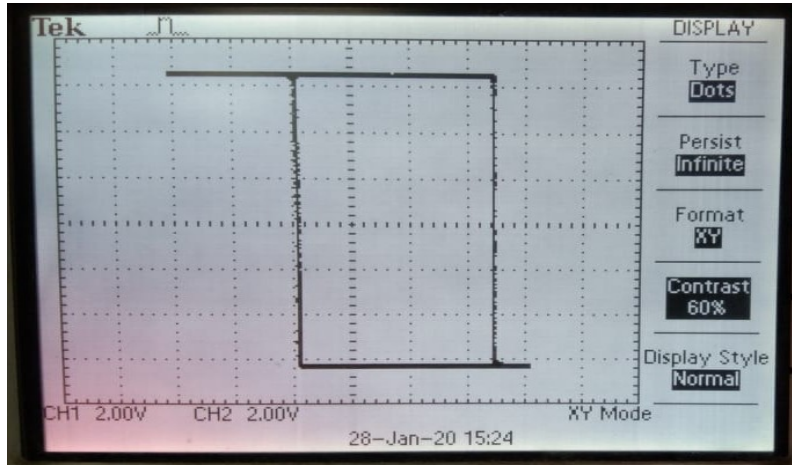


Figure 7: V_o versus V_i relationship for $V_a = 0V$

The observed value of $V_{TH} = +4.8V$ and $V_{TL} = -1.8V$

2.2 Astable multivibrator

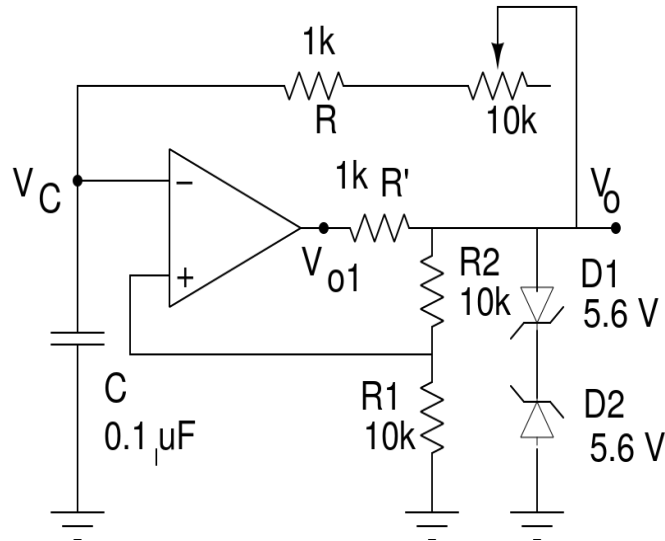


Figure 8: Astable multivibrator

The actual resistance of resistors shown in fig 8 are, $R_1 = 9.7k$, $R_2 = 9.82k$, $R' = 0.99k$, $R = 0.96k$

(A) For maximum time period :

The resistance between V_C and V_O comes out to be $10.73k\Omega$

Since here $V_a = 0V$,

$$V_{TH} = -V_{TL} \equiv V_T \quad (14)$$

The period of oscillation is

$$T = 2\tau \log\left(\frac{V_m + V_T}{V_m - V_T}\right) \quad \text{where } \tau = RC \quad (15)$$

$$T = 2(10.73k)(0.1\mu) \log\left(\frac{6.72 + 3.4}{6.72 - 3.4}\right) \quad (16)$$

$$\boxed{T = 2.39ms} \quad (17)$$

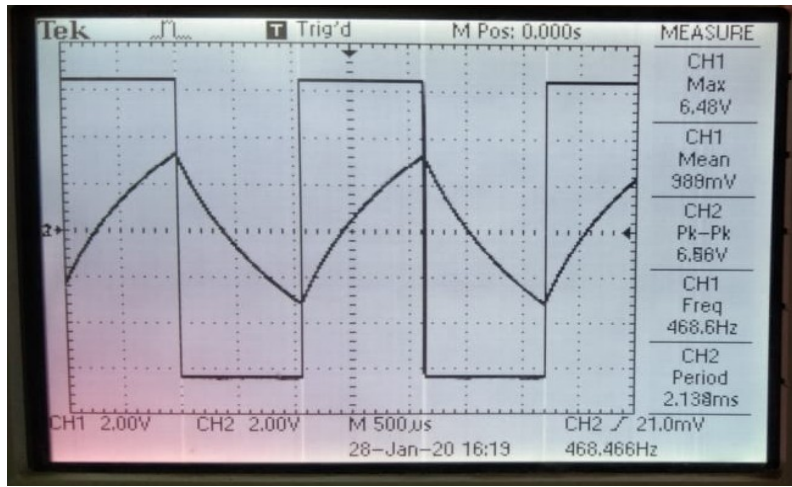


Figure 9: Output for maximum time period

The observed maximum time period is **T = 2.138ms**

(B) For minimum time period :

The resistance between V_C and V_O comes out to be **0.96k Ω**

Again, the period of oscillation is given by

$$T = 2\tau \times \log\left(\frac{V_m + V_T}{V_m - V_T}\right) \quad \text{where } \tau = RC \quad (18)$$

$$T = 2 \times (0.96k) \times (0.1\mu) \times \log\left(\frac{6.72 + 3.4}{6.72 - 3.4}\right) \quad (19)$$

$$\boxed{T = 214\mu s} \quad (20)$$

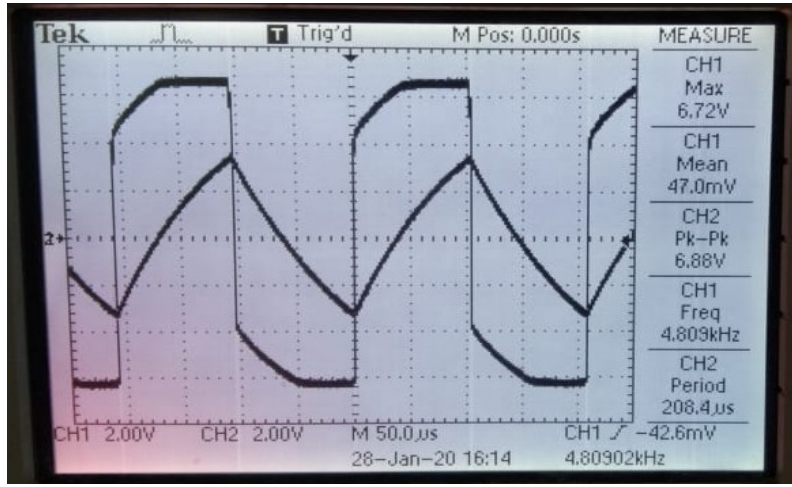


Figure 10: Output for minimum time period

The observed minimum time period is $T = 208.4\mu s$

2.3 Monostable multivibrator

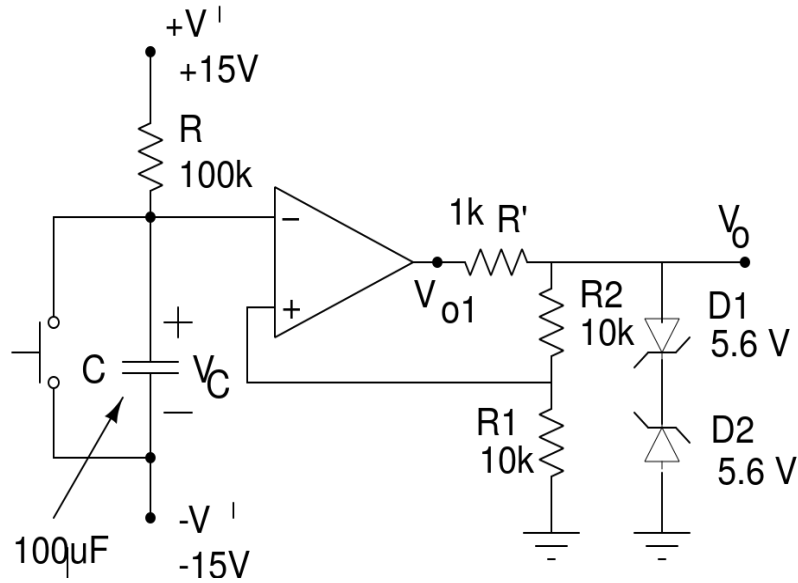


Figure 11: Monostable multivibrator

The actual resistance of resistors shown in fig 11 are, $R_1 = 9.7k$, $R_2 = 9.82k$, $R' = 0.99k$, $R = 100.5k$

The voltage to which the capacitor charges is $2V' = 10.6V$

The output pulse width, T is given by the expression

$$\begin{aligned}
 T &= RC \times \log\left(\frac{V'}{V' - V_{TH}}\right) \\
 &= (100.5k) \times (100\mu) \times \log\left(\frac{5.3}{5.3 - 3.4}\right) \\
 \boxed{T = 10.25s}
 \end{aligned} \tag{21}$$

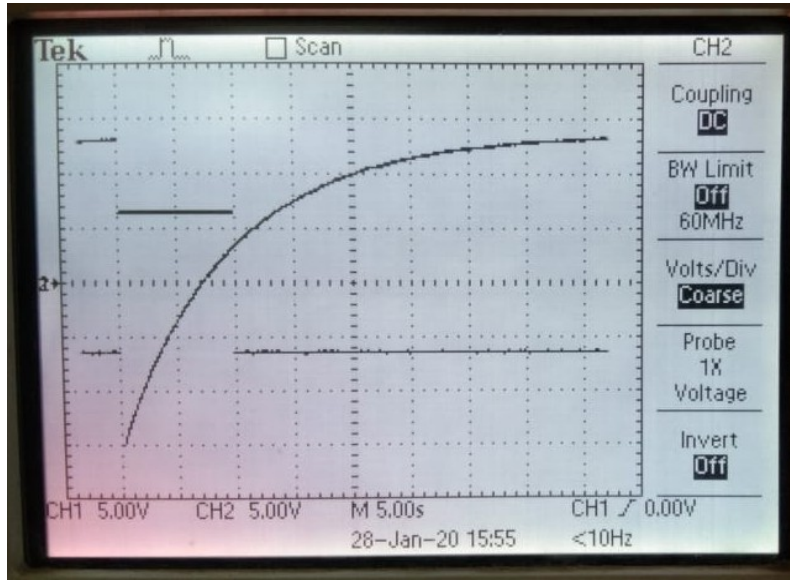


Figure 12: Waveforms of V_- and V_o

The observed pulse width comes out to be $\mathbf{T = 10.1s}$

References

- [1] Scmitt supporting document
https://moodle.iitb.ac.in/pluginfile.php/302403/mod_resource/content/0/schmitt_astable_support.pdf