

# EE 214: Experiment - 1

## Characterization of CMOS Transistor

Hitesh Kandala, 180070023

January 25, 2020

### 1 Overview of the Experiment and Setup:

In this experiment we characterized a CMOS inverter. To characterize a CMOS inverter, we have done a DC (or steady state behaviour) characterization by measuring its transfer characteristics and output characteristics and also an AC (or transient behaviour) characterization and measured the inverter delay and its dependence on the power supply, and observed the currents drawn from the power supply.

- For measuring the characteristics, we used *IC MM74C04 - 4*


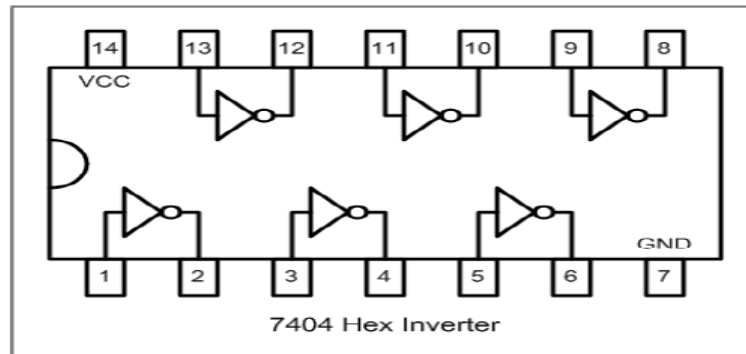


Figure 1: Pin diagram of the MM74C04

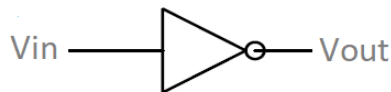- The DC transfer characteristics are determined by calculating the output voltage with varying the input voltage from 0V to 5V from a single inverter in the IC.



- The output characteristics is the variation of output voltage with output current, we measured output voltage VS output current via a potentiometer connected to the output terminal for two different cases a)Output is high b)Output is low

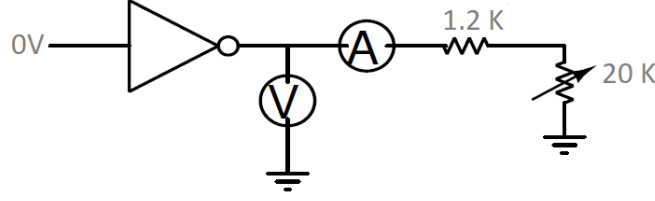


Figure 2: Output characteristics when output is high

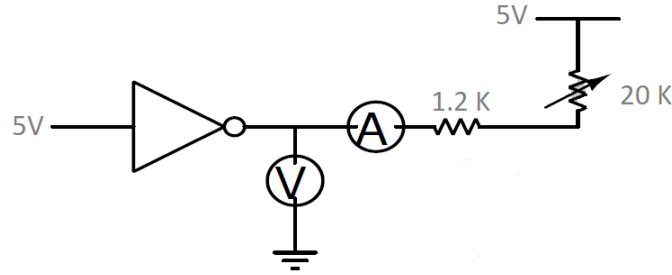


Figure 3: Output characteristics when output is low

- The delay of an inverter is measured using a **Ring Oscillator** which is a delay oscillator consisting of odd number of inverters connected in a ring. The period of the oscillation is twice the sum of all the inverter delays. Also the delay depends on its load capacitance.

$$d = k_0 + \tau_{inv} \frac{C_{load}}{C_{in}} \text{ (in seconds)} \quad (1)$$

$k_0$  is a constant and  $\tau_{inv}$  is an inverter parameter delay(d) can be adjusted into  $\tau_{inv}$  units and the equation becomes

$$d^* = p_{inv} + \frac{C_{load}}{C_{in}} \text{ (in } \tau_{inv} \text{ units)} \quad (2)$$

We used 17 inverters in ring oscillator and calculated period(in s) of the oscillation for different loads(open inverters), the period is related to delay by

$$\tau \times (34p_{inv} + (32 + (2 \times (1 + AdditionalOutputLoad)))) \quad (3)$$

The Additional Output Load is the number of open inverters connected to the ring Oscillator

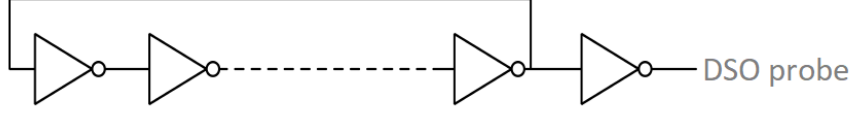


Figure 4: Ring oscillator circuit with default load (=2)

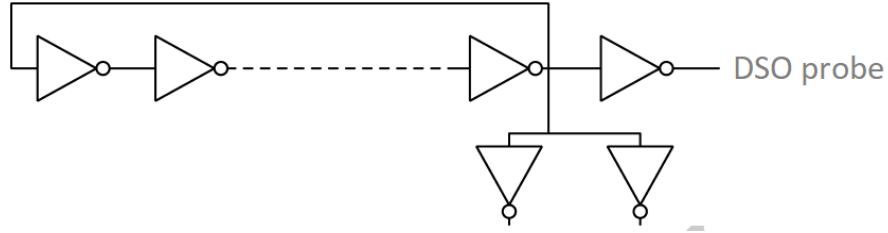


Figure 5: Ring oscillator circuit with additional 3-inverter load

- The delay of an inverter varies as the supply voltage is varied. We measured the ring oscillator period(to estimate the delay) for a fixed load(=2) at each voltage from 3V to 5V in 0.5 steps

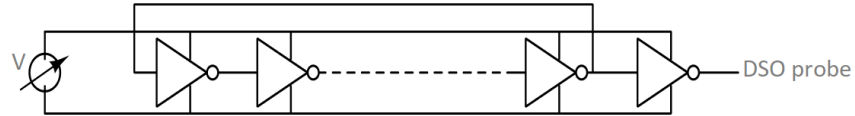


Figure 6: Test circuit for measuring the delay as a function of supply voltage

- Whenever an inverter output switches from low to high, current is drawn from the power supply. The current drawn is approximately a triangular pulse whose width is essentially the delay of the gate. We connected a resistor ( $R=1$ ) in series with ground path to observe this. The voltage across the resistor is same as the current through it.


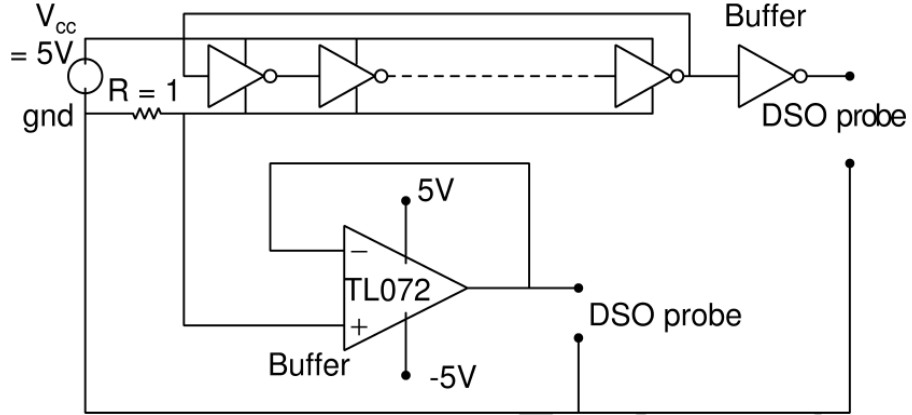


Figure 7: Circuit diagram for switching current measurement

## 2 Observations


### 2.1 Transfer Characteristics

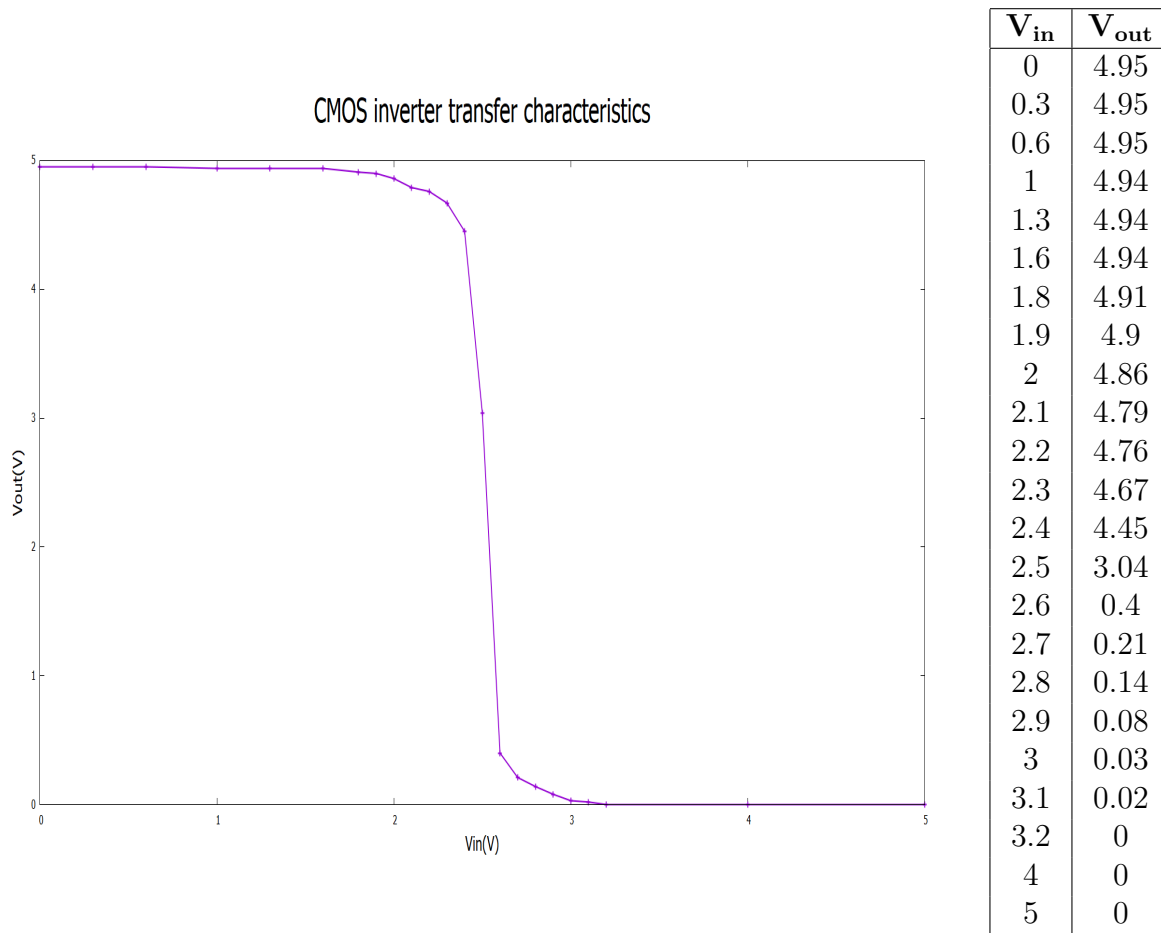

Therefore, from the graph we get that the switching point of CMOS inverter is around 2.5 V

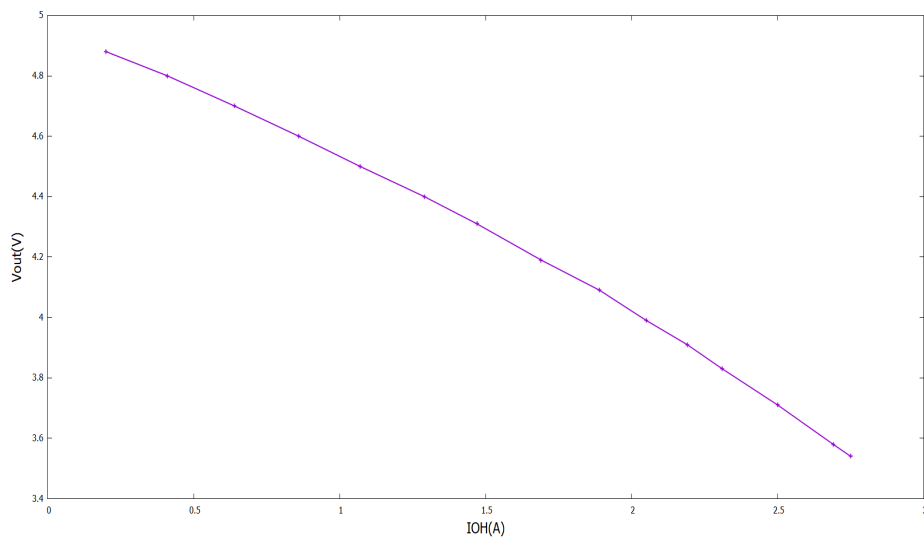
## 2.2 Output Characteristics

Output Characteristics when output is high




$V_{in}$	$V_{out}$
4.88	0.2
4.8	0.41
4.7	0.64
4.6	0.86
4.5	1.07
4.4	1.29
4.31	1.47
4.19	1.69
4.09	1.89
3.99	2.05
3.91	2.19
3.83	2.31
3.71	2.5
3.58	2.69
3.54	2.75

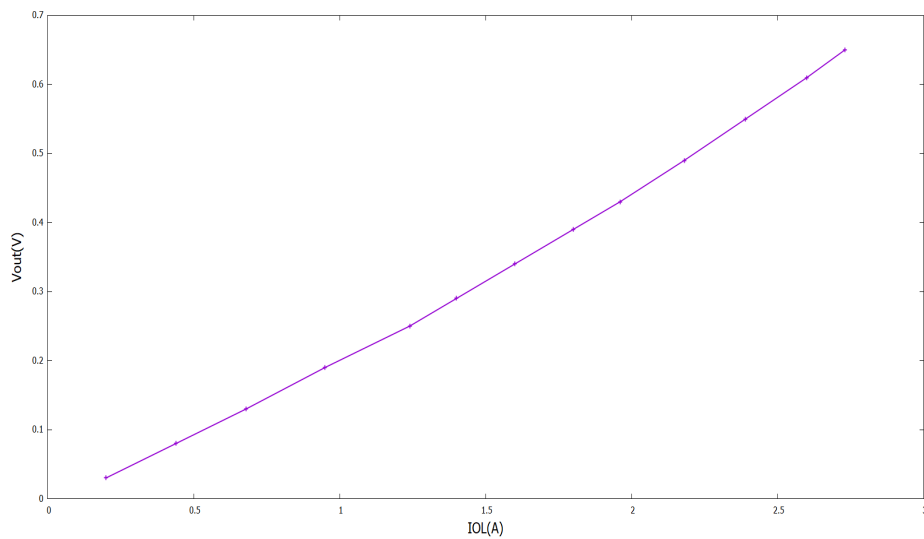Output Characteristics when output is low



$V_{in}$	$V_{out}$
0.03	0.2
0.08	0.44
0.13	0.68
0.19	0.95
0.25	1.24
0.29	1.4
0.34	1.6
0.39	1.8
0.43	1.96
0.49	2.18
0.55	2.39
0.61	2.6
0.65	2.73

## 2.3 Delay of the Inverter

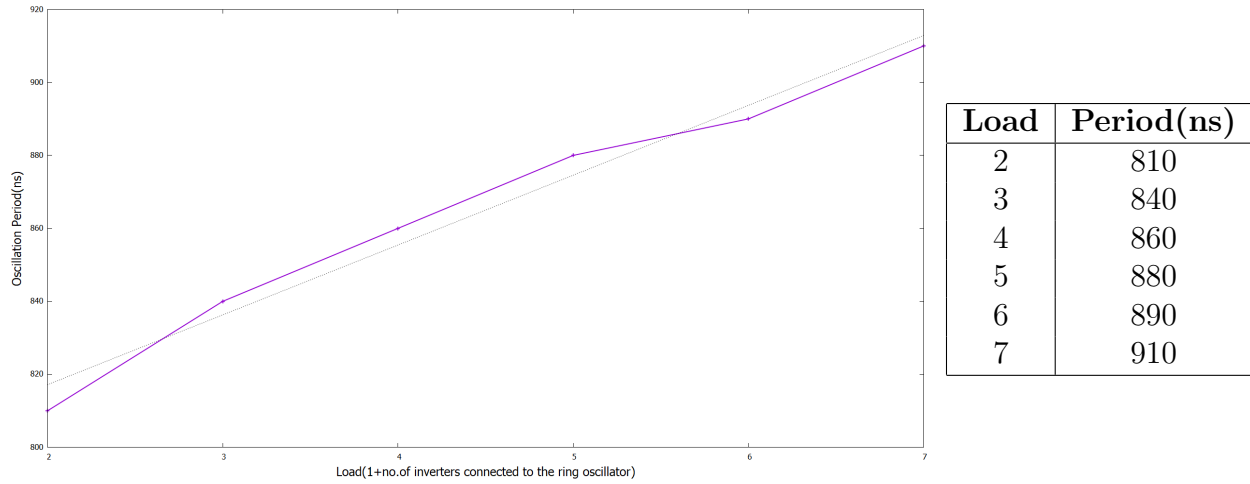

Slope and intercept of the best fit line are 19.14 n and 778.86 n respectively

The period of the ring oscillator is given by:

$$\tau \times (34p_{inv} + (32 + (2 \times (1 + AdditionalOutputLoad)))) \quad (4)$$

measured in seconds.

The slope of the above graph gives us  $\tau_{inv} = 9.57 \text{ ns}$ ,  $p_{inv}$  comes out to be 1.39


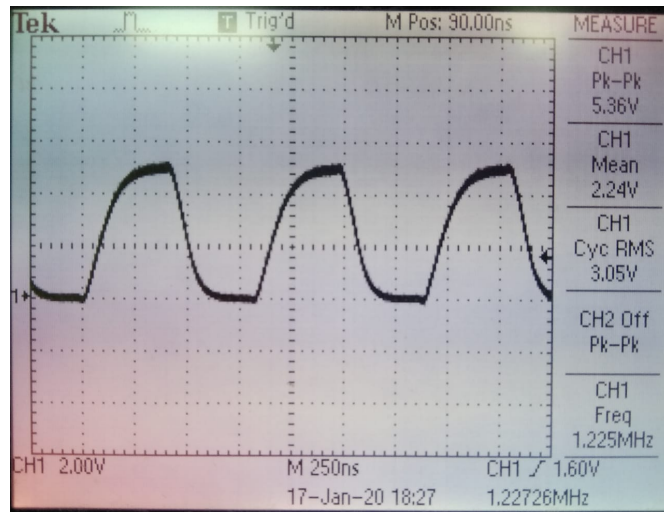



Figure 12: ring-oscillator output with load = 2
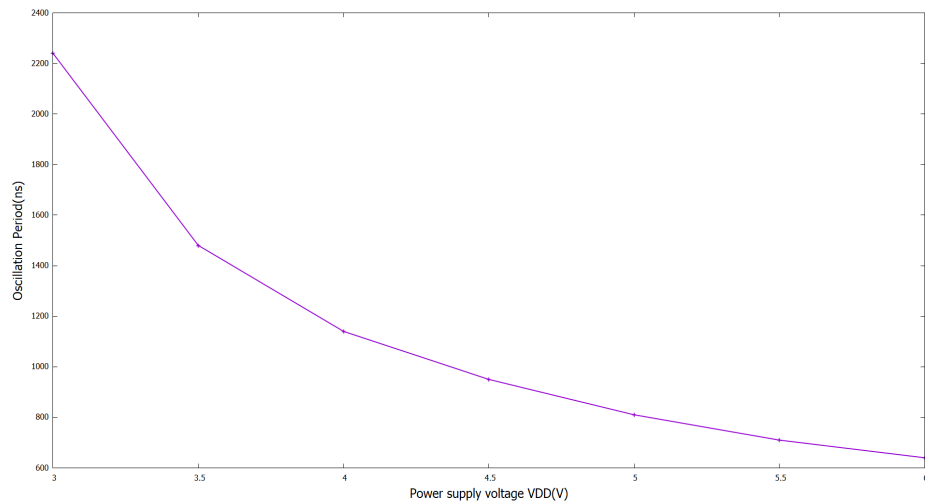
## 2.4 Dependence of Delay with supply voltage



V <sub>DD</sub>	Period(ns)
3	2240
3.5	1480
4	1140
4.5	950
5	810
5.5	710
6	640

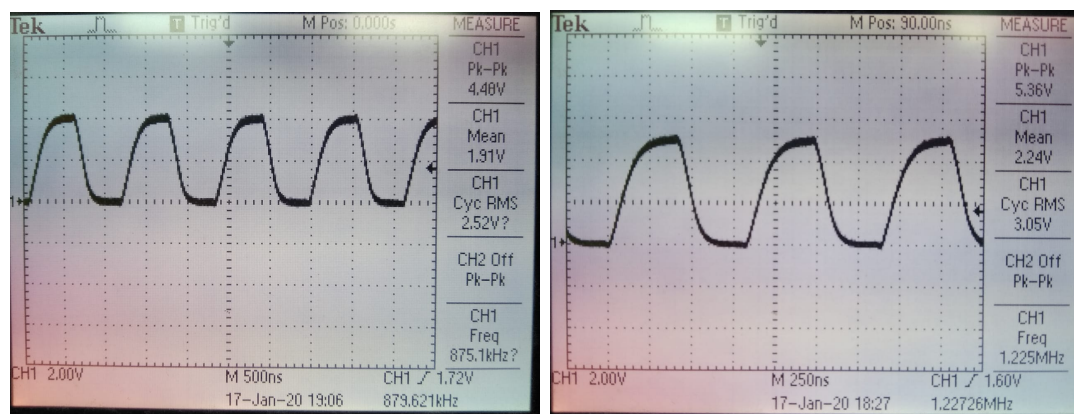As evident from the plot, delay decreases with increase in power supply



(a) Ring-oscillator output at supply voltage = 4V (b) Ring-oscillator output at supply voltage = 5V

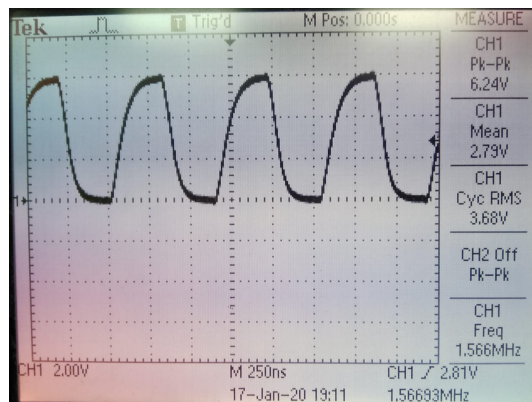


Figure 15: Ring-oscillator output at supply voltage = 6V



## 2.5 Switching current through the power supply

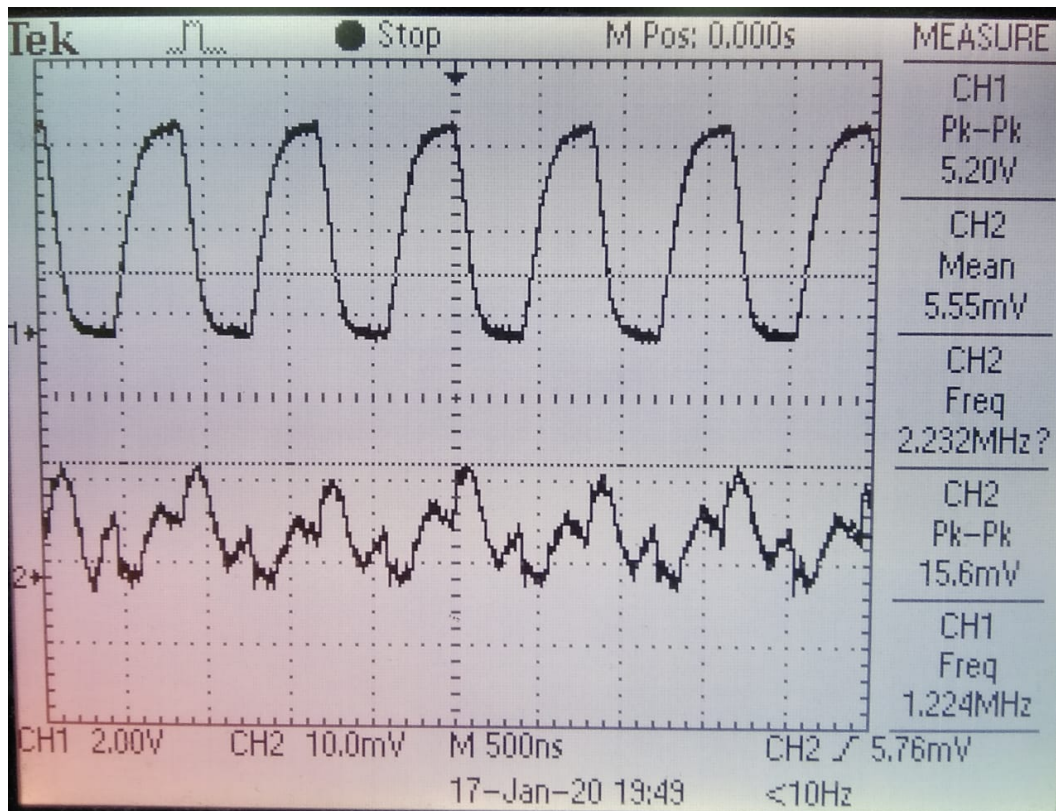


Figure 16: ring-oscillator output and voltage across the  $1\Omega$  resistance

As evident from the figure, the average and peak value of switching current are  $5.55mV$  and  $15.6mV$  respectively.